

VLSI Design

Concurrent Statements for Combinational
Logic

J Färber

SS2026

Contents

Concurrent Statements for Combinational Logic	2
Learning Objectives	2
Introductory Example: 4-Bit Up-Counter	3
Schematic Symbol and RTL Conceptual Diagram	3
Function	3
WITH ... SELECT — Selected Signal Assignment	4
Syntax	4
Completeness: WHEN OTHERS	4
Example: 2-to-1 Multiplexer	4
Example: 7-Segment Decoder (bin2seg)	5
Modeling Truth Tables with WITH ... SELECT	6
Concatenating Inputs into a Select Vector	6
Example: 1-Bit Full Adder as Truth Table	7
WHEN ... ELSE — Conditional Signal Assignment	8
Syntax	8
Priority of Conditions	9
Example: 2-to-1 Multiplexer	9
Example: Priority Encoder	10
WITH ... SELECT vs. WHEN ... ELSE	11
Outlook: Synchronous Logic	12
Summary	12
Reference	12

Concurrent Statements for Combinational Logic

Learning Objectives

After completing this unit, you will be able to:

- Use WITH ... SELECT to map discrete input values to output values
- Model any combinational truth table by concatenating inputs into a vector
- Use WHEN ... ELSE to describe conditional signal assignments with priority
- Select the appropriate construct for a given design situation
- Apply both constructs as the exclusive modelling tool for combinational and synchronous logic

Introductory Example: 4-Bit Up-Counter

Schematic Symbol and RTL Conceptual Diagram

Function

 


Figure 1: Behaviour - Timing Diagram

WITH ... SELECT — Selected Signal Assignment

Syntax

Referring to [Mea25], chap. 5.2

```
WITH select_expression SELECT
  target_signal <= value_a WHEN choice_1,
                 value_b WHEN choice_2,
                 value_c WHEN choice_3,
                 value_default WHEN OTHERS;
```

Figure 2: Selected Signal Assignment - Conceptual Diagram

- All choices are evaluated **simultaneously** — there is no priority
- WHEN OTHERS is mandatory: it covers every value not listed explicitly
- The select expression must be of a discrete type (`std_ulogic_vector`, `unsigned`, `signed`, `enumeration`)

Completeness: WHEN OTHERS

For an N-bit `std_ulogic_vector` there are 9^N possible values because each bit can be '0', '1', 'U', 'X', 'Z', 'W', 'L', 'H', or '-'. Even a 1-bit signal has 9 states — WHEN OTHERS is therefore always required to make the assignment complete.

In synthesis, only '0' and '1' matter. In simulation, WHEN OTHERS covers uninitialised ('U') and unknown ('X') states, making errors visible immediately.

Example: 2-to-1 Multiplexer

Referring to [Mea25], chap. 5.1

 


Figure 3: mux2to1 — Schematic Symbol

The function table of mux2to1:

sel_i	y_o
0	b_i
1	a_i

ARCHITECTURE truthtable **OF** mux2to1 **IS**

BEGIN

```
WITH sel_i SELECT
  y_o <= a_i WHEN '1',
        b_i WHEN OTHERS;
```

END truthtable;

Example: 7-Segment Decoder (bin2seg)

bin2seg maps a 4-bit binary input to the active-low 7-segment encoding of the hexadecimal digits 0 to F. This is a truth table with 16 rows — exactly the use case `WITH ... SELECT` is designed for.

Segment labelling:	Encoding: seg_o = "gfedcba"
0	active-low: '0' = segment ON

5 1	
--- < 6	
4 2	

3	

ENTITY bin2seg **IS**

PORT (

```
  bin_i : IN  std_ulogic_vector(3 DOWNTO 0);
  seg_o : OUT std_ulogic_vector(6 DOWNTO 0)  -- gfedcba, active-low
);
```

END bin2seg;

ARCHITECTURE rtl **OF** bin2seg **IS**

```

BEGIN

WITH bin_i SELECT
  seg_o <=
    "1000000" WHEN "0000", -- 0
    "1111001" WHEN "0001", -- 1
    "0100100" WHEN "0010", -- 2
    "0110000" WHEN "0011", -- 3
    "0011001" WHEN "0100", -- 4
    "0010010" WHEN "0101", -- 5
    "0000010" WHEN "0110", -- 6
    "1111000" WHEN "0111", -- 7
    "0000000" WHEN "1000", -- 8
    "0010000" WHEN "1001", -- 9
    "1111111" WHEN OTHERS; -- all segments off

END rtl;

```

Each row of the truth table maps directly to one WHEN clause. The synthesiser infers a combinational decoder — no intermediate signals, no boolean equations required.

Modeling Truth Tables with WITH ... SELECT

Concatenating Inputs into a Select Vector

Example: 2-input arbitrary function

```

-- Inputs: a, b (single bits)
-- Concatenation: a & b results in a 2-Bit-Vector

WITH (a & b) SELECT
  y <= '1' WHEN "10", -- a=1, b=0
        '0' WHEN "00", -- a=0, b=0
        '0' WHEN "01", -- a=0, b=1
        '0' WHEN "11", -- a=1, b=1
        '0' WHEN OTHERS;

```

Example: 3-input Majoriy Gate

```

-- 3-input Majoriy Gate
-- provides a y = '1' if and only if at least two of its three inputs are '1'.
-- Inputs: a, b, c (single bits)
-- Concatenation: a & b results in a 2-Bit-Vektor

WITH (

```

When a circuit has multiple single-bit inputs, they can be **concatenated** into one `std_ulogic_vector` and used as the select expression. This directly maps a truth table to VHDL.

```
SIGNAL inputs_s : std_ulogic_vector(N-1 DOWNTO 0);

inputs_s <= in_a & in_b & in_c;  -- concatenate N inputs

WITH inputs_s SELECT
  output_s <= value_0 WHEN "000",
             value_1 WHEN "001",
             ...
             value_default WHEN OTHERS;
```

Similarly, multiple output bits can be concatenated into one vector signal and split apart after the assignment:

```
SIGNAL outputs_s : std_ulogic_vector(1 DOWNTO 0);

WITH inputs_s SELECT
  outputs_s <= "00" WHEN "000",
             "01" WHEN "001",
             ...
             "00" WHEN OTHERS;

out_a <= outputs_s(1);
out_b <= outputs_s(0);
```

Example: 1-Bit Full Adder as Truth Table

A 1-bit full adder has three inputs (`a_i`, `b_i`, `ci_i`) and two outputs (`sum_o`, `co_o`). The complete truth table has $2^3 = 8$ rows.

ci_i	b_i	a_i	co_o	sum_o
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

```

ENTITY add1 IS
  PORT (
    a_i : IN std_ulogic;
    b_i : IN std_ulogic;
    ci_i : IN std_ulogic;
    sum_o : OUT std_ulogic;
    co_o : OUT std_ulogic
  );
END add1;

ARCHITECTURE truthtable OF add1 IS

  SIGNAL inputs_s : std_ulogic_vector(2 DOWNTO 0);
  SIGNAL outputs_s : std_ulogic_vector(1 DOWNTO 0); -- (co_o, sum_o)

BEGIN

  inputs_s <= ci_i & b_i & a_i;

  WITH inputs_s SELECT
    outputs_s <=
      " " WHEN "000", -- 0+0+0 = , co=
      " " WHEN "001", -- 1+0+0 = , co=
      " " WHEN "010", -- 0+1+0 = , co=
      " " WHEN "011", -- 1+1+0 = , co=
      " " WHEN "100", -- 0+0+1 = , co=
      " " WHEN "101", -- 1+0+1 = , co=
      " " WHEN "110", -- 0+1+1 = , co=
      " " WHEN "111", -- 1+1+1 = , co=
      " " WHEN OTHERS;

  co_o <= outputs_s(1);
  sum_o <= outputs_s(0);

END truthtable;

```

This approach scales to any combinational circuit: write the truth table, concatenate inputs, enumerate outputs. No boolean minimisation required — the synthesiser optimises automatically.

WHEN ... ELSE — Conditional Signal Assignment

Syntax

```

target_signal <= value_a WHEN condition_1 ELSE
  value_b WHEN condition_2 ELSE
  value_default;


```

Figure 4: Conditional Signal Assignment - Conceptual Diagram

- Each branch is evaluated in order — **the first true condition wins**
- The final ELSE clause is mandatory: it covers all remaining cases
- The statement executes **concurrently** — it models a combinational network, not a sequential program

Priority of Conditions

 Because conditions are checked from top to bottom, WHEN ... ELSE naturally models **priority logic**: a condition listed earlier takes precedence over all conditions listed below it.



This priority behaviour maps directly to a **priority multiplexer** in hardware — useful whenever one input must override others.

Example: 2-to-1 Multiplexer

The mux2to1 from the previous section can also be written with WHEN ... ELSE. Comparing both architectures makes the difference in readability concrete:

```

-- WITH ... SELECT (previous section) – reads like a lookup table
WITH sel_i SELECT
  y_o <= a_i WHEN '1',
    b_i WHEN OTHERS;

-- WHEN ... ELSE – reads like a condition chain, identical hardware
y_o <= a_i WHEN sel_i = '1' ELSE
  b_i;

```

Both architectures produce exactly the same synthesised circuit. WHEN ... ELSE allows arbitrary boolean expressions as conditions, not just equality with a single signal.

Compare also with the boolean-equation architecture from Lecture 2:

```

-- boolean equation (Lecture 2)
y_o <= (sel_i AND a_i) OR (NOT sel_i AND b_i);

```

All three architectures are equivalent — only readability differs.

Example: Priority Encoder

A 4-to-2 priority encoder asserts the index of the **highest-priority** active input. Input x_i (3) has highest priority.

x_i	y_o
1 x x x	11
0 1 x x	10
0 0 1 x	01
0 0 0 1	00

$x_i(3)$ overrides all

The overlapping x entries make this table impossible to model with WITH ... SELECT (which requires mutually exclusive, fully enumerated values). WHEN ... ELSE encodes priority directly through the order of conditions:

```

ENTITY priority42 IS
  PORT (
    x_i      : IN  std_ulogic_vector(3 DOWNTO 0);
    y_o      : OUT std_ulogic_vector(1 DOWNTO 0);

  );
END priority42;

ARCHITECTURE rtl OF priority42 IS
  BEGIN

```

```
y_o <=
```

```
END rtl;
```

The order of conditions encodes priority — swapping two lines changes which input wins. This is the key capability that `WITH ... SELECT` lacks.

WITH ... SELECT vs. WHEN ... ELSE

	WITH ... SELECT	WHEN ... ELSE
Conditions	Discrete values of one expression	Arbitrary boolean expressions
Priority	No priority — all choices equal	First matching condition wins
Completeness	WHEN OTHERS required	Final ELSE required
Best for	Truth tables, decoders, multiplexers	Priority logic, range checks, complex conditions
Typical use	bin2seg, mux, full adder	Priority encoder, address decoder

Rule of thumb:

- Use `WITH ... SELECT` when the output depends on the **value** of a single expression — reads like a lookup table
- Use `WHEN ... ELSE` when the output depends on **conditions** that may overlap or carry priority

Both constructs produce equivalent hardware when conditions are mutually exclusive.

Outlook: Synchronous Logic

The same two constructs — WITH ... SELECT and WHEN ... ELSE — are used in the next Lecture to model **synchronous (clocked) circuits** such as registers and counters.

Summary

- WITH ... SELECT assigns a value based on the **enumerated cases** of one expression — no priority, reads like a truth table
- WHEN ... ELSE assigns a value based on **ordered conditions** — the first true condition wins (priority behaviour)
- Both constructs are **concurrent** — they model hardware, not software
- Any combinational truth table can be modelled by **concatenating inputs** into a select vector and listing all output combinations
- WHEN OTHERS / final ELSE are mandatory for completeness
- The same constructs extend to synchronous logic in Lecture 4

Next Lecture: Synchronous Logic: registers, counters, and clocked circuits with WHEN ... ELSE

Reference

- [Mea25] Mealy, B., Tappero, F.: *Free Range VHDL*, 2025 — Chapter 5