

# VLSI Design

Sequential Circuit Design

J Färber

SS2026

## Contents

<b>Sequential Circuit Design</b>	<b>2</b>
Learning Objectives . . . . .	2
D-Type Flip-Flop / D-Type Register . . . . .	3
Schematic Symbol . . . . .	3
Function . . . . .	3
Timing Diagram . . . . .	3
VHDL Model . . . . .	4
Design Rules for Synchronous Digital Circuit Design . . . . .	5
Falling Edge Detector . . . . .	6
Schematic Symbol and RTL Diagram . . . . .	6
Timing Diagram . . . . .	6
Truth Table . . . . .	6
VHDL Model . . . . .	7
Simulation Environment . . . . .	7
Counter . . . . .	10
Schematic Symbol and RTL Diagram . . . . .	10
Function . . . . .	10
VHDL Model . . . . .	11
Simulation Environment . . . . .	12
Prototype Test Environment . . . . .	14
Shift Register . . . . .	15
Schematic Symbol . . . . .	15
Function . . . . .	15
VHDL Model . . . . .	15
Simulation Environment . . . . .	17
Pseudo-Random Binary Sequence Generator . . . . .	19
Schematic . . . . .	19
Function . . . . .	19
VHDL Model . . . . .	20
Simulation Environment . . . . .	21
Summary . . . . .	23
Reference . . . . .	23

# Sequential Circuit Design

## Learning Objectives

After completing this unit, you will be able to:


- Describe the function of a D-type flip-flop and its role as the fundamental storage element in synchronous circuits
- State and apply the three mandatory design rules for synchronous digital circuits
- Model a D-type flip-flop and an n-bit register using WHEN ... ELSE in VHDL
- Design an edge detector and derive its output logic from a truth table of flip-flop states
- Decompose a synchronous counter into next-state logic and state register, and model both using WHEN ... ELSE
- Model a shift register and describe the shift-right operation as a concatenation of flip-flop outputs
- Describe the structure of a Linear Feedback Shift Register and its application as a pseudo-random sequence generator
- Write a synchronous testbench with clock generation, asynchronous reset, and self-checking ASSERT statements

## D-Type Flip-Flop / D-Type Register

### Schematic Symbol

### Function

### Timing Diagram

 

**Figure 1:** D-Type Flip-Flop - Timing Behaviour

## VHDL Model

```
ENTITY d_ff IS
  PORT (clk_i : IN std_ulogic;
        rst_ni : IN std_ulogic;

        d_i : IN std_ulogic;
        q_o : OUT std_ulogic
        );
END d_ff;
```

```
ARCHITECTURE rtl OF d_ff IS
```

```
BEGIN
```

```
  dflipflop : q_o <=
```

```
END rtl;
```

```
ENTITY dregen IS
  PORT (clk_i : IN std_ulogic;
        rst_ni : IN std_ulogic;
```

```
        d_i : IN std_ulogic;
        q_o : OUT std_ulogic
        );
```

```
END dregen;
```

```
ARCHITECTURE rtl OF dregen IS
```

```
BEGIN
```


```
  dregister : q_o <=
```

```
END rtl;
```
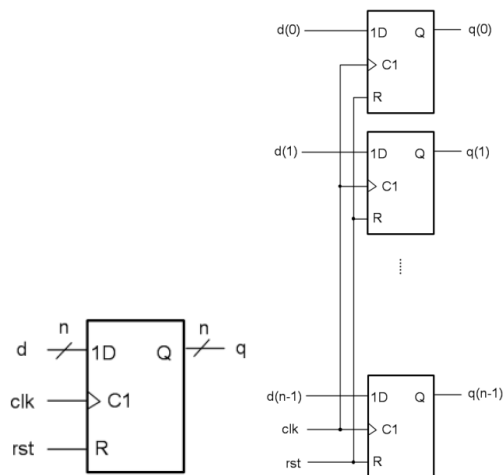
## Design Rules for Synchronous Digital Circuit Design


The general design rules for designing synchronous circuits are mandatory:

- There is only one common clock signal  $clk$ , which is connected to all clock inputs of  $n$ -bit storage elements
- A clock signal is never linked via logic elements.
- Each synchronous module has a reset signal, never connected via additional logic.




## Falling Edge Detector

### Schematic Symbol and RTL Diagram

 

### Timing Diagram

 

**Figure 2:** Falling Edge Detector - Waveform Diagram

### Truth Table

q1	q0	fall_o
0	0	0
0	1	0
1	0	1
1	1	0

$fall\_o = f(q1, q0)$

## VHDL Model

```
ENTITY falling_edge_detector IS
  PORT (
    clk_i   : IN  std_ulogic;
    rst_ni  : IN  std_ulogic;
    x_i     : IN  std_ulogic;
    fall_o  : OUT std_ulogic
  );
END falling_edge_detector;

ARCHITECTURE rtl OF falling_edge_detector IS

  SIGNAL q0, q1 : std_ulogic;           -- D-Type Flip-Flop outputs

BEGIN

  dflipflop_0 : q0 <=

  dflipflop_1 : q1 <=

  output_logic : fall_o <=

END rtl;
```

## Simulation Environment

```
ENTITY t_falling_edge_detector IS
END t_falling_edge_detector;

ARCHITECTURE tbench OF t_falling_edge_detector IS

  COMPONENT falling_edge_detector
  PORT (
    clk_i   : IN  std_ulogic;
    rst_ni  : IN  std_ulogic;
    x_i     : IN  std_ulogic;
    fall_o  : OUT std_ulogic);
  END COMPONENT;

  -- definition of a clock period
  CONSTANT period : time := 10 ns;
  -- switch for clock generator
  SIGNAL clken_p  : boolean := true;

  -- component ports
  SIGNAL clk_i   : std_ulogic;
  SIGNAL rst_ni  : std_ulogic;
  SIGNAL x_i     : std_ulogic;
  SIGNAL fall_o  : std_ulogic;
```

```
BEGIN -- tbench

-- Module Under Verification
MUV : ENTITY work.falling_edge_detector(rtl)
  PORT MAP (
    clk_i => clk_i,
    rst_ni => rst_ni,
    x_i    => x_i,
    fall_o => fall_o);

-- clock generation
clock_p : PROCESS
BEGIN
  WHILE clken_p LOOP
    clk_i <= '0'; WAIT FOR period/2;
    clk_i <= '1'; WAIT FOR period/2;
  END LOOP;
  WAIT;
END PROCESS;

-- initial reset, always necessary at the beginning of a simulation
reset : rst_ni <= '0', '1' AFTER period;

stimuli_p : PROCESS
BEGIN

-----
-- wait until asynchronous reset is deactivated
-----

-----

-----
-- create a low-active pulse over a no. of clock periods
-----

-- assign a '1' to x_i

-- set input to '0' ...
-- ... for a no. of periods

-- assign a '1' to form a
-- low active input pulse

-----
```

```

-----
-- create a low-active pulse over a no. of clock periods
-----
x_i <= '1';           -- assign a '1' to x_i
WAIT FOR period;

x_i <= '0';           -- set input to '0' ...
WAIT UNTIL rising_edge(clk_i);
WAIT UNTIL falling_edge(clk_i);
-----
-- Observer: check, if fall_o is assigned to '1' for one clock period
-----
ASSERT fall_o = '1' REPORT "Error: Expected fall_o = '1' !" SEVERITY failure;
WAIT UNTIL falling_edge(clk_i);
ASSERT fall_o = '0' REPORT "Error: Expected fall_o = '0' !" SEVERITY failure;
WAIT FOR 6 * period;  -- ... for a no. of periods


x_i <= '1';           -- assign a '1' to form a
WAIT FOR 3 * period; -- low active input pulse
-----

clken_p <= false;    -- switch clock generator off

WAIT;                -- suspend proces
END PROCESS;


END tbench;

```

 


**Figure 3:** - Simulation Result

## Counter

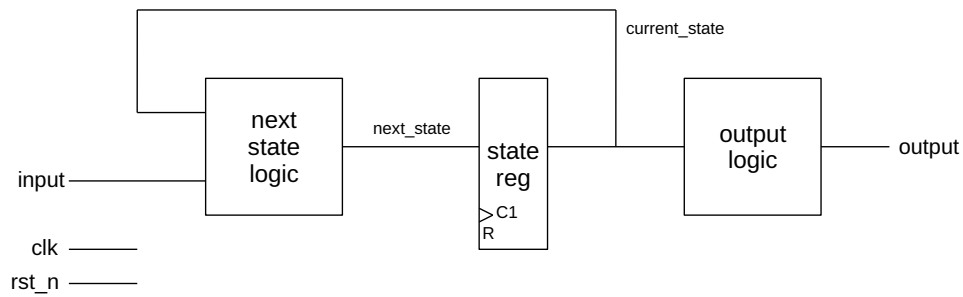

**Figure 4:** Synchronous Sequential Circuit - Conceptual Diagram

## Schematic Symbol and RTL Diagram

 

## Function

inputs			outputs	
rst_ni	clk_i	en_pi	q(t+1)	Remark
0	-	-	0	Asynchronous reset active
1	0	-	q(t)	Store count value
1	1	-	q(t)	Store count value
1	^	0	q(t)	Store count value
1	^	1	q(t) + 1	count = count + 1

## VHDL Model

```
LIBRARY IEEE;
USE IEEE.std_logic_1164.ALL;
USE IEEE.numeric_std.ALL;

ENTITY cntupen IS
  PORT (clk_i   : IN  std_ulogic;
        rst_ni  : IN  std_ulogic;
        en_pi   : IN  std_ulogic;
        count_o : OUT std_ulogic_vector(3 DOWNTO 0)
        );
END cntupen;

ARCHITECTURE rtl OF cntupen IS

  -- datatype unsigned is defined in package numeric_std
  SIGNAL next_state, current_state : unsigned(3 DOWNTO 0);

BEGIN

  -- package numeric_std overloads operator '+'
  -- for arguments of different types, here: unsigned and integer

  incrementer : next_state <=

  -- synthesisable construct of a d-type register with synchronous enable

  state_register : current_state <=

  -- type conversion from unsigned to std_ulogic_vector necessary

  counter_output : count_o <=

END rtl;
```

## Simulation Environment

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY t_cntupen IS
END t_cntupen;

ARCHITECTURE tbench OF t_cntupen IS

  COMPONENT cntupen
  PORT (
    clk_i   : IN  std_ulogic;
    rst_ni  : IN  std_ulogic;
    en_pi   : IN  std_ulogic;
    count_o : OUT std_ulogic_vector(3 DOWNTO 0));
  END COMPONENT;

  -- definition of a clock period
  CONSTANT period : time := 10 ns;
  -- switch for clock generator
  SIGNAL clken_p : boolean := true;

  -- component ports
  SIGNAL clk_i   : std_ulogic;
  SIGNAL rst_ni  : std_ulogic;
  SIGNAL en_pi   : std_ulogic;
  SIGNAL count_o : std_ulogic_vector(3 DOWNTO 0);

BEGIN -- tbench

  -- component instantiation
  MUV : ENTITY work.cntupen(rtl)
  PORT MAP (
    clk_i  => clk_i,
    rst_ni => rst_ni,
    en_pi  => en_pi,
    count_o => count_o);

  -- clock generation
  clock_p : PROCESS

  -- initial reset, always necessary at the beginning of a simulation
  -----
  -- Following a verification plan:
  -----
  -- 1. t = 0 ns: activate asynchronous reset
  -- 2. t = 10 ns: deactivate asynchronous reset
  -----
  reset :

```

```

stimuli_p : PROCESS

BEGIN

-----
-- ... continuing with the verification plan:
-----

WAIT UNTIL rst_ni = '1';           -- wait until asynchronous reset ...
                                   -- ... is deactivated
-----

-----
-- 2. activate enable
-- 3. Wait for a full counting cycle
-----

en_pi <= '1';                       -- activate enable input en_pi
WAIT FOR 15 * period;               -- wait for at least one count cycle
ASSERT count_o = X"F" REPORT "Error: Expected count_o = F !" SEVERITY failure;
-----

WAIT FOR 5 * period;               -- wait for a no. of count values
                                   -- then ...
-----

-----
-- 4. After another five periods: Deactivate Enable
-----

en_pi <= '0';                       -- .... deactivate enable input en_pi
WAIT FOR 3 * period;
-----

-----
-- 5. After another three periods: Activate Enable
-- 6. Simulate another complete counting cycle
-----

en_pi <= '1';                       -- activate enable input en_pi
WAIT FOR 15 * period;               -- wait for at least one count cycle
ASSERT count_o = X"3" REPORT "Error: Expected count_o = F !" SEVERITY failure;
-----

-----
-- 7. Switch off the clock generator
-----


clken_p <= false;                   -- switch clock generator off

WAIT;                               -- suspend proces

END PROCESS;


END tbench;

```

 


**Figure 5:** 4-Bit Binary Up Counter with Enable - Simulation Result


**Prototype Test Environment**

 

**Figure 6:** 4-Bit Binary Up Counter with Enable - DE1 Test Environment

 


**Figure 7:** 4-Bit Binary Up Counter with Enable - Quartus RTL Viewer

 

**Figure 8:** 4-Bit Binary Up Counter with Enable - Quartus Technology Map Viewer


## Shift Register

### Schematic Symbol

 

**Figure 9:** 4-Bit Shift Register - Schematic

### Function

 

**Figure 10:** 4-Bit Shift Right Register - Simulation Result

### VHDL Model

```

ENTITY sreg4 IS
  PORT (clk_i : IN std_ulogic;
        rst_ni : IN std_ulogic;          -- asynchronous L-active reset
        ser_i  : IN std_ulogic;          -- serial data stream input
        ser_o  : OUT std_ulogic;         -- serial data stream output
        par_o  : OUT std_ulogic_vector(3 DOWNTO 0) -- parallel data output
  );
END sreg4;

ARCHITECTURE rtl OF sreg4 IS

  SIGNAL q : std_ulogic_vector(3 DOWNTO 0);
  SIGNAL d : std_ulogic_vector(3 DOWNTO 0);

  -- continuous on next page ...

```

**BEGIN**

## Simulation Environment

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY t_sreg4 IS
END ENTITY t_sreg4;

ARCHITECTURE tbench OF t_sreg4 IS

    -- component ports
    SIGNAL clk_i : std_ulogic;
    SIGNAL rst_ni : std_ulogic;
    SIGNAL ser_i : std_ulogic;
    SIGNAL ser_o : std_ulogic;
    SIGNAL par_o : std_ulogic_vector(3 DOWNTO 0);

    -- definition of a clock period
    CONSTANT period : time := 20 ns;
    -- switch for clock generator
    SIGNAL clken_p : boolean := true;

BEGIN -- ARCHITECTURE tbench

    -- component instantiation
    DUT : ENTITY work.sreg4
        PORT MAP (
            clk_i => clk_i,
            rst_ni => rst_ni,
            ser_i => ser_i,
            ser_o => ser_o,
            par_o => par_o);

    -- clock generation
    clock_p : PROCESS
    BEGIN
        WHILE clken_p LOOP
            clk_i <= '0'; WAIT FOR period/2;
            clk_i <= '1'; WAIT FOR period/2;
        END LOOP;
        WAIT;
    END PROCESS;

    -- initial reset, always necessary at the beginning OF a simulation
    reset : rst_ni <= '0', '1' AFTER period;

    -- process for stimuli generation
    stimuli_p : PROCESS

    BEGIN

        WAIT UNTIL rst_ni = '1';           -- wait until asynchronous reset ...
        -- ... is deactivated

        -- serial input data stream
        ser_i <= '0';
        WAIT FOR period;
        ser_i <= '1';
        WAIT FOR period;
        ser_i <= '0';

```

```
WAIT FOR period;
ser_i <= '1';
WAIT FOR period;
-- check parallel output

-----

ser_i <= '0';
WAIT FOR 4 * period;
-- check parallel output

-----

-- serial input data stream
ser_i <= '1';
WAIT FOR period;
ser_i <= '0';
WAIT FOR period;
ser_i <= '1';
WAIT FOR period;
ser_i <= '0';
WAIT FOR period;
-- check parallel output

-----

WAIT FOR 4 * period;


-----

clken_p <= false;           -- switch clock generator off

WAIT;
END PROCESS;
```

## Pseudo-Random Binary Sequence Generator

### Schematic

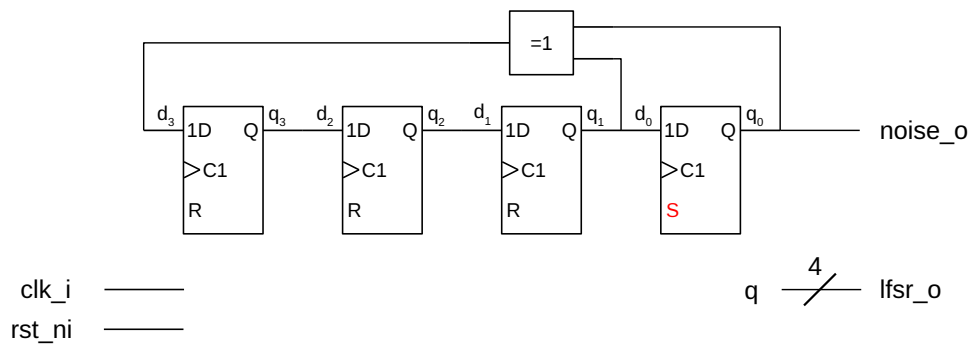

**Figure 11:** 4-bit Linear-Feedback Shift Register (Fibonacci) - Schematic

### Function

## VHDL Model

```
ENTITY lfsr4 IS
  PORT (clk_i   : IN  std_ulogic;
        rst_ni  : IN  std_ulogic;      -- asynchronous L-active reset
        en_pi   : IN  std_ulogic;      -- '1' -> enable data generation
        lfsr_o  : OUT std_ulogic_vector(3 DOWNTO 0); -- lfsr data output
        noise_o : OUT std_ulogic;      -- lfsr serial data stream output
        eoc_po  : OUT std_ulogic);     -- end of cycle notification:
-- provides '1' WHEN lfsr_o = "00 .. 01"
END lfsr4;

ARCHITECTURE fibonacci OF lfsr4 IS

  SIGNAL q : std_ulogic_vector(lfsr_o'length-1 DOWNTO 0); -- current state
  SIGNAL d : std_ulogic_vector(lfsr_o'length-1 DOWNTO 0); -- next state

BEGIN

  -- linear feedback
  feedback :

  -- next state logic
  next_state_logic :

  -- state_register :
  state_register :

  -- parallel output
  parallel_out :

  -- serial output
  serial_out :

  -- end of cycle notification
  end_of_cycle :

END fibonacci;
```

## Simulation Environment

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY t_lfsr4 IS
END ENTITY t_lfsr4;

ARCHITECTURE tbench OF t_lfsr4 IS

    -- component ports
    SIGNAL clk_i    : std_ulogic;
    SIGNAL rst_ni   : std_ulogic;
    SIGNAL en_pi    : std_ulogic;
    SIGNAL lfsr_o   : std_ulogic_vector(3 DOWNTO 0);
    SIGNAL noise_o  : std_ulogic;
    SIGNAL eoc_po   : std_ulogic;

    -- definition of a clock period
    CONSTANT period : time    := 20 ns;
    -- switch for clock generator
    SIGNAL clken_p  : boolean := true;

BEGIN -- ARCHITECTURE tbench

    -- component instantiation
    DUT : ENTITY work.lfsr4(fibonacci)
        PORT MAP (
            clk_i  => clk_i,
            rst_ni => rst_ni,
            en_pi  => en_pi,
            lfsr_o => lfsr_o,
            noise_o => noise_o,
            eoc_po => eoc_po);

    -- clock generation
    clock_p : PROCESS
    BEGIN
        WHILE clken_p LOOP
            clk_i <= '0'; WAIT FOR period/2;
            clk_i <= '1'; WAIT FOR period/2;
        END LOOP;
        WAIT;
    END PROCESS;

    -- initial reset, always necessary at the beginning OF a simulation
    reset : rst_ni <= '0', '1' AFTER period;

    -- process for stimuli generation
    stimuli_p : PROCESS

    BEGIN


        WAIT UNTIL rst_ni = '1';           -- wait until asynchronous reset ...
        -- ... is deactivated

```

```
clken_p <= false;           -- switch clock generator off

WAIT;
END PROCESS;

END ARCHITECTURE tbench;
```

 

**Figure 12:** 4-Bit Linear Feedback Shift Register - Simulation Result

## Summary

- The fundamental storage element is the **D-type flip-flop** — it samples its input `d_i` on the **rising edge** of `clk_i` and holds the value until the next clock edge
- Three **mandatory design rules** govern all synchronous circuits: one shared clock, no combinational logic on clock paths, reset never gated through additional logic
- An **n-bit register** is a collection of D flip-flops sharing clock and reset — modelled as a single `WHEN ... ELSE` statement with `rising_edge(clk_i)`
- An **edge detector** cascades two flip-flops to compare the current and previous signal value — the output logic is a combinational function of both flip-flop states, derived from a truth table
- A **synchronous counter** separates next-state logic (incrementer) from the state register — both parts are modelled with `WHEN ... ELSE`, using unsigned arithmetic from `ieee.numeric_std`
- A **shift register** implements serial-to-parallel conversion by chaining flip-flop outputs — the shift operation is expressed as a vector concatenation
- A **Linear Feedback Shift Register (LFSR)** generates a pseudo-random binary sequence through XOR feedback — a compact source of test stimuli and noise signals

**Next Lecture:** Finite State Machine Design: Moore-type FSMs with enumerated state types and state diagrams

## Reference

- [Mea25] Mealy, B., Tappero, F.: *Free Range VHDL*, 2025
  - Chapters 4.4, 6.5, 7, 13