

VLSI Design

VHDL Fundamentals

J Färber

SS2026

Contents

VHDL Fundamentals	2
Learning Objectives	2
VHDL Design Unit: Entity and Architecture	2
Library and Package Declarations	2
ENTITY Declaration	3
ARCHITECTURE Body	3
Data Types	4
std_ulogic – Single-Bit Signal	4
std_ulogic_vector – Multi-Bit Signal	5
Internal Signals	5
Arithmetic Types from ieee.numeric_std	6
Arithmetic Operations	6
Type Conversion Overview	7
Shift Operations	8
Design Hierarchy	8
Module Hierarchy	8
Component Instantiation	9
Naming Conventions for Files	10
Testbench	10
Testbench Structure	10
Combinational Testbench	11
Prototype Test Environment	12
Summary	13
Reference	13

VHDL Fundamentals

Learning Objectives

After completing this unit, you will be able to:

- Describe a digital circuit using VHDL ENTITY and ARCHITECTURE
- Use the fundamental data types `std_logic` and `std_logic_vector`
- Declare internal SIGNALs and use them in concurrent assignments
- Use arithmetic types `unsigned` and `signed` from `ieee.numeric_std`
- Perform type conversions between `std_logic_vector`, `unsigned`, and `signed`
- Structure a design into a hierarchy of modules using component instantiation
- Write a self-checking testbench with stimuli generation and ASSERT

VHDL Design Unit: Entity and Architecture

Every VHDL design consists of two parts:

- The **ENTITY** describes the interface — inputs and outputs (ports)
- The **ARCHITECTURE** describes the function — what the circuit does

Think of the entity as the circuit symbol, and the architecture as the schematic inside it.

 


Figure 1: mux2to1 - Schematic Symbol

Library and Package Declarations

Before every VHDL file, include the standard IEEE library:

```
LIBRARY IEEE;  
USE IEEE.std_logic_1164.ALL;
```

For arithmetic operations, also include:

```
USE IEEE.numeric_std.ALL;
```

ENTITY Declaration

Referring to [Mea25], chap. 3.1 Entity

The entity declares all ports with their direction and data type:

```
ENTITY mux2to1 IS
  PORT (
    a_i  : IN  std_ulogic;  -- data input A (selected when sel_i = '1')
    b_i  : IN  std_ulogic;  -- data input B (selected when sel_i = '0')
    sel_i : IN  std_ulogic;  -- select: '1' → a_i, '0' → b_i
    y_o  : OUT std_ulogic
  );
END mux2to1;
```

Port directions:

Direction	Meaning
IN	Input — can only be read inside the architecture
OUT	Output — can only be assigned inside the architecture

Naming convention: input ports end with `_i`, output ports with `_o`.

ARCHITECTURE Body

Referring to [Mea25], chap. 3.3 Architecture

Figure 2: mux2to1 - Schematic

The architecture defines the circuit behaviour. All statements inside BEGIN ... END execute **concurrently** — they model hardware, not a sequential program.

```
ARCHITECTURE equation OF mux2to1 IS
BEGIN
    y_o <= (sel_i AND a_i) OR (NOT sel_i AND b_i);
END equation;
```

The label after OF must match the entity name exactly. The label after IS (here: equation) names the architecture. Multiple architectures can exist for the same entity.

Data Types

std_ulogic — Single-Bit Signal

std_ulogic models a single digital signal. The most important values in synthesis and simulation:

Value	Meaning
'0'	Logic zero
'1'	Logic one
'U'	Uninitialised (simulation only)
'X'	Unknown / conflict (simulation only)

std_u`logic`_vector – Multi-Bit Signal

An array of `std_ulogic` elements — used for buses and registers:

```
SIGNAL data : std_ulogic_vector(7 DOWNTO 0); -- 8-bit bus
SIGNAL addr : std_ulogic_vector(3 DOWNTO 0); -- 4-bit address
SIGNAL reg  : std_ulogic_vector(7 DOWNTO 0); -- 8-bit bus
```

Index convention: (n-1 DOWNTO 0) - MSB on the left, LSB on the right.

Assigning individual bits:

```
data(7) <= '1'; -- assign MSB
data    <= "10110100"; -- assign all 8 bits (binary literal)
data    <= X"B4"; -- same value as hex literal
address <= X"A"; -- assign a 4-Bit value
data    <= (OTHERS => '0'); -- assign all bits to '0'
```

Concatenation with &:

```
data <= "0000" & addr; -- prepend four zeros to addr
reg  <= '1' & data(7 DOWNTO 1); -- shift right, injecting a '1' at MSB
reg  <= data(0) & data(7 DOWNTO 1); -- rotate right
```

Internal Signals

Signals declared in the architecture declaration area are internal wires — they connect concurrent statements and instances (see chapter: Design Hierarchy) within the architecture.

The `mux2to1` can use an internal signal to hold the inverted select, making the boolean equation more readable:

```
ARCHITECTURE rtl OF mux2to1 IS

    SIGNAL not_sel_s : std_ulogic; -- inverted select

BEGIN

    not_sel_s <= NOT sel_i;
    y_o      <= (sel_i AND a_i) OR (not_sel_s AND b_i);

END rtl;
```

Both architectures (equation and `rtl`) describe the same circuit — the synthesiser produces identical hardware from either.

Arithmetic Types from `ieee.numeric_std`

For arithmetic operations (addition, subtraction, comparison), `std_ulogic_vector` must be converted to an arithmetic type.

Type	Meaning	Example
<code>unsigned</code>	Unsigned binary number	"0101" = 5
<code>signed</code>	Two's complement signed number	"1101" = -3

Arithmetic Operations

```

LIBRARY IEEE;
USE IEEE.std_logic_1164.ALL;
USE IEEE.numeric_std.ALL;

ENTITY add4 IS
  PORT (a_i : IN std_ulogic_vector(3 DOWNTO 0); -- operand a
        b_i : IN std_ulogic_vector(3 DOWNTO 0); -- operand b
        sum_o : OUT std_ulogic_vector(3 DOWNTO 0); -- sum
        co_o : OUT std_ulogic; -- carry out
        );
END add4;

ARCHITECTURE rtl OF adder IS

  SIGNAL a, b, sum : unsigned(3 DOWNTO 0);

BEGIN

  a <= unsigned(a_i); -- convert from std_ulogic_vector
  b <= unsigned(b_i);
  sum <= a + b; -- arithmetic addition
  y_o <= std_ulogic_vector(sum); -- convert back

END rtl;

```

signed arithmetic works the same way — and integer literals can be mixed directly with signed or unsigned operands:

```


SIGNAL a, b : std_ulogic_vector(3 DOWNTO 0);
SIGNAL sa, sb : signed(3 DOWNTO 0);
SIGNAL sc : signed(7 DOWNTO 0);
SIGNAL sd : signed(7 DOWNTO 0);

sc <= sa + sb; -- addition, result assigned to wider signal
sc <= sa + 5; -- signed + integer literal
sc <= sa + (-5); -- negative integer literal
sc <= -5 + sa; -- swapped argument order is allowed
sc <= sa - sb; -- subtraction
sd <= sa * sb; -- multiplication: result width = sa'length + sb'length

```

Multiplication result width: `sa` and `sb` are 4 bits each — the product can be up to 8 bits wide, so `sd` must be declared as `signed(7 DOWNTO 0)` to hold the full result without truncation.

Type Conversion Overview

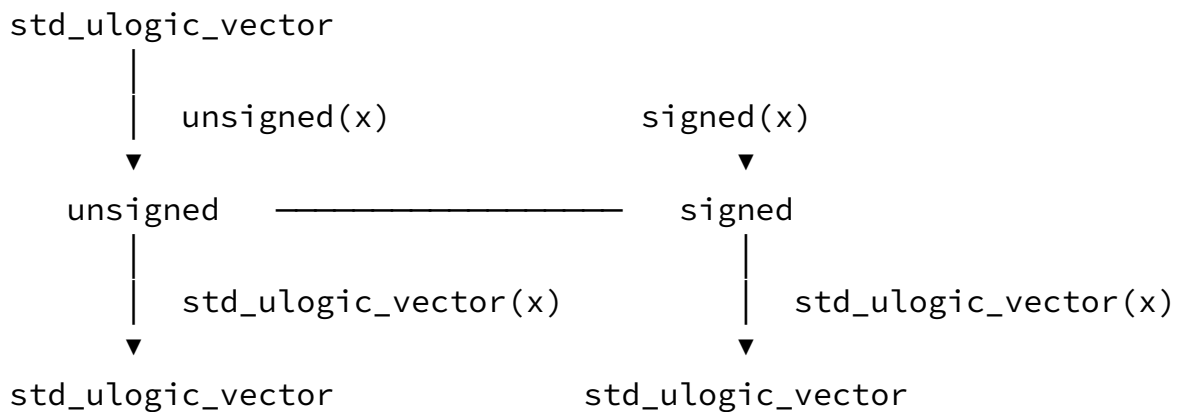

Common conversion patterns:

```

-- std_ulogic_vector → unsigned → arithmetic → std_ulogic_vector
SIGNAL a_u   : unsigned(3 DOWNTO 0);
SIGNAL sum_u : unsigned(3 DOWNTO 0);

a_u  <= unsigned(a_i);
sum_u <= a_u + 1;
y_o  <= std_ulogic_vector(sum_u);
  
```

The **'length** attribute returns the bit width of a signal and avoids hardcoding numbers:

```

SIGNAL a, b   : std_ulogic_vector(3 DOWNTO 0);
SIGNAL sa, sb : signed(3 DOWNTO 0);
SIGNAL sc     : signed(7 DOWNTO 0);
SIGNAL ua, ub : unsigned(3 DOWNTO 0);
SIGNAL i      : integer RANGE -30 TO 30;

sa <= signed(a);           -- typecast: std_ulogic_vector → signed
a  <= std_ulogic_vector(sa); -- typecast: signed → std_ulogic_vector
ua <= unsigned(a);        -- typecast: std_ulogic_vector → unsigned

i <= to_integer(sa);       -- convert signed → integer (e.g. for indexing)
sa <= to_signed(-2, sa'length); -- convert integer → signed, width from 'length

sc <= resize(sa, sc'length); -- sign extension: 4-bit signed → 8-bit signed
  
```

resize and sign extension: for `signed`, `resize` to a wider type replicates the MSB (sign bit) into the new upper bits — this preserves the two's complement value. For `unsigned`, the upper bits are filled with zeros.

INTEGER RANGE: the `RANGE` constraint limits the integer value range. This allows the

synthesiser to infer a minimal number of bits rather than allocating a full 32-bit register.

Shift Operations

`shift_right` and `shift_left` from `ieee.numeric_std` perform **arithmetic** shifts on signed or unsigned signals:

```
sa <= shift_right(sa, 1); -- arithmetic right shift by 1 bit (÷ 2)
sa <= shift_left(sa, 1); -- arithmetic left shift by 1 bit (× 2)
```

Arithmetic vs. logical shift: for signed, `shift_right` fills the vacated MSB positions with the **sign bit**, preserving the two's complement value. `shift_left` fills from the right with '0'. These differ from the VHDL operators `srl/sll`, which always fill with '0'.

Design Hierarchy

Referring to [Mea25], chap. 9.1

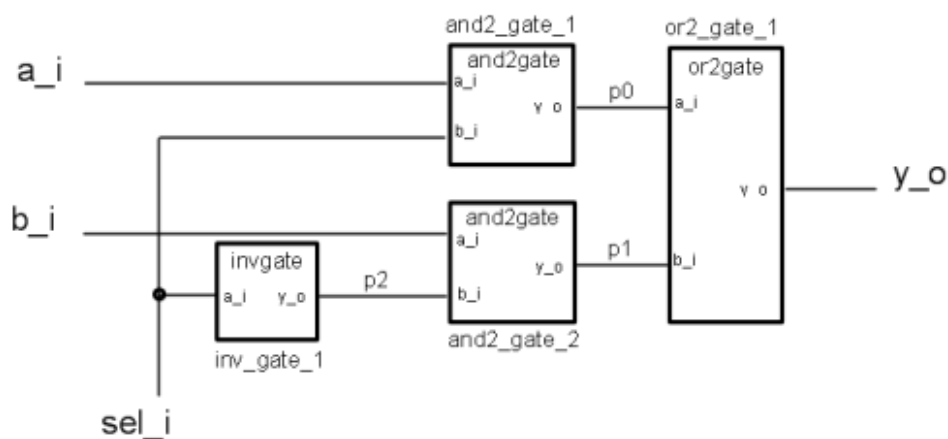


Figure 3: 2-to-1 Multiplexer - Schematic

Module Hierarchy

ENTITY (ARCHITECTURE)

t_mux2to1(tbench)	de1_mux2to1(structure)
mux2to1(structure)	mux2to1(structure)
and2gate(equation)	and2gate(equation)
or2gate(equation)	or2gate(equation)
invgate(equation)	invgate(equation)

Filenames

```
|  
+---src  
    and2gate_equation.vhd  
    invgate_equation.vhd  
    or2gate_equation.vhd  
    mux2to1_structure.vhd  
    t_mux2to1.vhd  
    de1_mux2to1_structure.vhd
```

Component Instantiation

```
LIBRARY IEEE;  
USE IEEE.std_logic_1164.ALL;  
  
ENTITY mux2to1 IS  
    PORT (a_i : IN std_ulogic;  
          b_i : IN std_ulogic;  
          sel_i : IN std_ulogic;  
          y_o : OUT std_ulogic  
          );  
END mux2to1;  
  
ARCHITECTURE structure OF mux2to1 IS  
  
    COMPONENT invgate  
        PORT (  
            a_i : IN std_ulogic;  
            y_o : OUT std_ulogic);  
    END COMPONENT;  
  
    COMPONENT and2gate  
        PORT (  
            a_i : IN std_ulogic;  
            b_i : IN std_ulogic;  
            y_o : OUT std_ulogic);  
    END COMPONENT;  
  
    COMPONENT or2gate  
        PORT (  
            a_i : IN std_ulogic;  
            b_i : IN std_ulogic;  
            y_o : OUT std_ulogic);  
    END COMPONENT;  
  
    SIGNAL wire0, wire1 : std_ulogic;  
    SIGNAL wire2 : std_ulogic;  
  
BEGIN  
  
    inv_gate_1 : invgate  
        PORT MAP (  
            a_i => sel_i,  
            y_o => wire2);
```

```

and2_gate_1 : and2gate
  PORT MAP (
    a_i => a_i,
    b_i => sel_i,
    y_o => wire0);

and2_gate_2 : and2gate
  PORT MAP (
    a_i => b_i,
    b_i => wire2,
    y_o => wire1);

or2_gate_1 : or2gate

END structure;

```

Naming Conventions for Files

File	Content
mux2to1_structure.vhd	Entity mux2to1, Architecture structure
t_mux2to1.vhd	Testbench entity t_mux2to1
de1_mux2to1_structure.vhd	Envelope for FPGA prototype testing

Testbench

A testbench is a VHDL file that instantiates the **Device Under Test (DUT)**, applies input stimuli, and observes outputs. The testbench entity has **no ports**.

Testbench Structure

 


Figure 4: 2-to-1 Multiplexer - Conceptual Diagram of a Test Bench

Combinational Testbench

The mux2to1 has three inputs — all $2^3 = 8$ combinations are tested, grouped by the select signal:

```

LIBRARY IEEE;
USE IEEE.std_logic_1164.ALL;

ENTITY t_mux2to1 IS
END t_mux2to1;

ARCHITECTURE tbench OF t_mux2to1 IS

    CONSTANT period : time := 10 ns;

    SIGNAL a_i      : std_ulogic;
    SIGNAL b_i      : std_ulogic;
    SIGNAL sel_i    : std_ulogic;
    SIGNAL y_o      : std_ulogic;

BEGIN

    -- Device Under Test
    DUT : ENTITY work.mux2to1(equation)
        PORT MAP (
            a_i => a_i,
            b_i => b_i,
            sel_i => sel_i,
            y_o => y_o
        );

    -- Stimuli
    stimuli_p : PROCESS
    BEGIN

        -- sel = '0' -> output follows b_i
        a_i <= '0'; b_i <= '0'; sel_i <= '0'; WAIT FOR period;
        ASSERT y_o = '0' REPORT "Error: sel=0, b=0 -> y/=0" SEVERITY failure;

        a_i <= '0'; b_i <= '1'; sel_i <= '0'; WAIT FOR period;
        ASSERT y_o = '1' REPORT "Error: sel=0, b=1 -> y/=1" SEVERITY failure;

        a_i <= '1'; b_i <= '0'; sel_i <= '0'; WAIT FOR period;
        ASSERT y_o = '0' REPORT "Error: sel=0, b=0 -> y/=0" SEVERITY failure;

        a_i <= '1'; b_i <= '1'; sel_i <= '0'; WAIT FOR period;
        ASSERT y_o = '1' REPORT "Error: sel=0, b=1 -> y/=1" SEVERITY failure;

        -- sel = '1' -> output follows a_i
        a_i <= '0'; b_i <= '0'; sel_i <= '1'; WAIT FOR period;
        ASSERT y_o = '0' REPORT "Error: sel=1, a=0 -> y/=0" SEVERITY failure;

        a_i <= '0'; b_i <= '1'; sel_i <= '1'; WAIT FOR period;
        ASSERT y_o = '0' REPORT "Error: sel=1, a=0 -> y/=0" SEVERITY failure;

        a_i <= '1'; b_i <= '0'; sel_i <= '1'; WAIT FOR period;
        ASSERT y_o = '1' REPORT "Error: sel=1, a=1 -> y/=1" SEVERITY failure;

        a_i <= '1'; b_i <= '1'; sel_i <= '1'; WAIT FOR period;
        ASSERT y_o = '1' REPORT "Error: sel=1, a=1 -> y/=1" SEVERITY failure;
    END PROCESS;

```

```

WAIT;    -- suspend process – simulation ends
END PROCESS;

END tbench;

```

Key elements of a combinational testbench:

Element	Purpose
CONSTANT period	Defines the time step between stimuli
stimuli_p PROCESS	Applies input values sequentially
WAIT FOR period	Holds input values for one time step
ASSERT	Self-checking: reports errors automatically
WAIT	Suspends the process – terminates simulation

Prototype Test Environment

 


Figure 5: Connection to Peripheral Elements

To test a module on the DE1 FPGA board, an **envelope architecture** connects the module ports to the physical pins of the board (switches, LEDs, 7-segment displays):

```

LIBRARY IEEE;
USE IEEE.std_logic_1164.ALL;

ENTITY de1_mux2to1 IS
    PORT (
        SW    : IN  std_ulogic_vector(2 DOWNTO 0);
        LEDR  : OUT std_ulogic_vector(3 DOWNTO 0)
    );
END de1_mux2to1;

ARCHITECTURE structure OF de1_mux2to1 IS

BEGIN

```

```

LEDR(0) <= SW(0);           -- show input a   on LED 0
LEDR(1) <= SW(1);           -- show input b   on LED 1
LEDR(2) <= SW(2);           -- show select   on LED 2

DUT : ENTITY work.mux2to1(equation)
  PORT MAP (
    a_i  => SW(0),
    b_i  => SW(1),
    sel_i => SW(2),
    y_o  => LEDR(3)           -- show result   on LED 3
  );

END structure;

```

The full module hierarchy for one design:

Simulation:

```

t_mux2to1(tbench)
  mux2to1(equation)

```

Prototype Testing:

```

de1_mux2to1(structure)
  mux2to1(equation)

```

Summary

- A VHDL design unit consists of an **ENTITY** (interface) and an **ARCHITECTURE** (function)
- All statements in an architecture execute **concurrently** — they model hardware, not software
- **std_ulogic** and **std_ulogic_vector** are the fundamental signal types
- **unsigned** and **signed** from `ieee.numeric_std` enable arithmetic
- **Type conversions** are explicit in VHDL — always convert before arithmetic
- **Internal signals** connect concurrent statements within an architecture
- **Component instantiation** builds design hierarchy with `ENTITY work.x PORT MAP`
- A **testbench** verifies correctness with stimuli, `WAIT FOR`, and `ASSERT`

Reference

- [Mea25] - Mealy, B., Tappero, F.: *Free Range VHDL*, 2025 — Chapters 2, 3, 4